

Aim: To verify Kirchhoff's Voltage Law

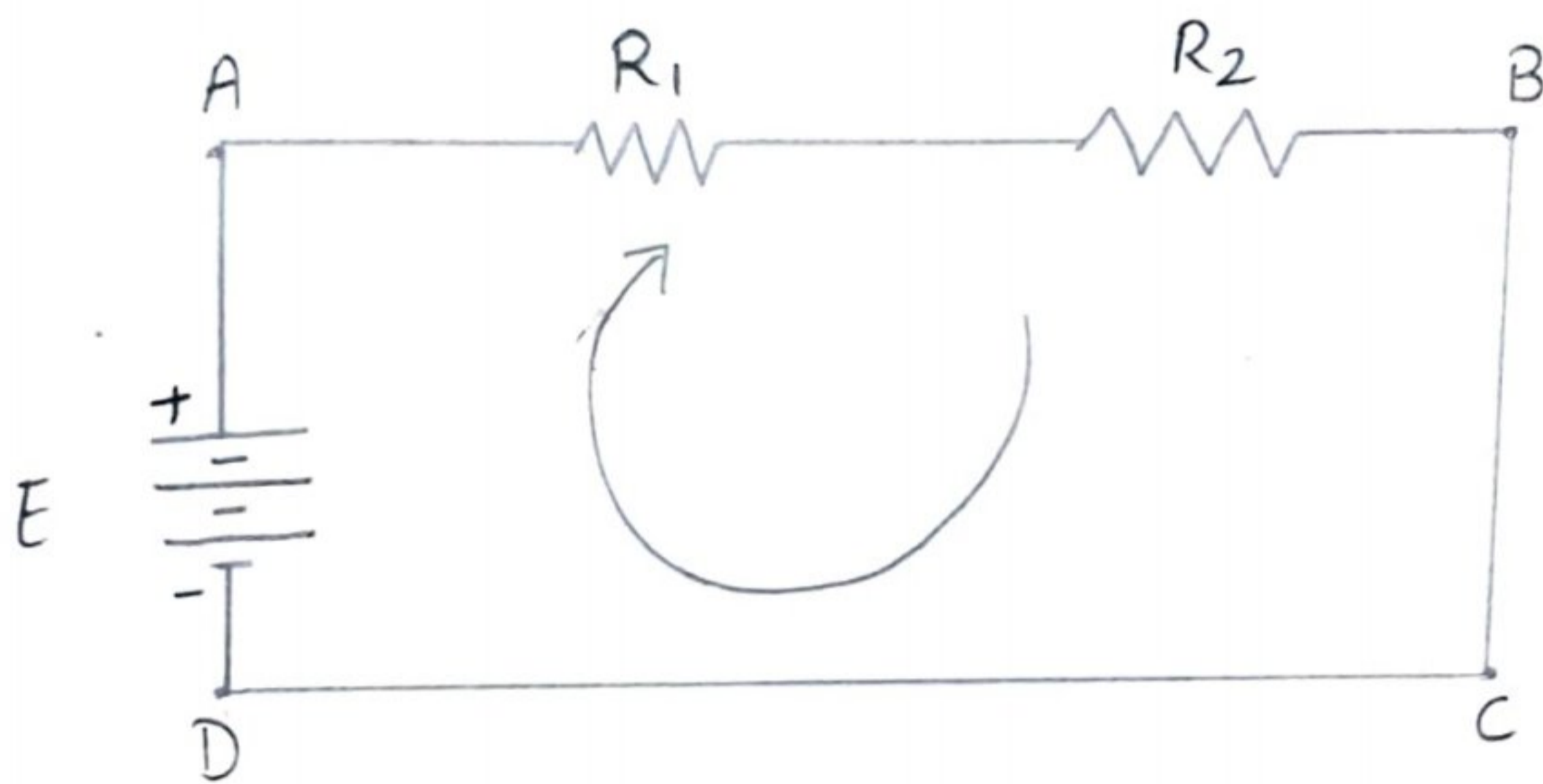


fig 1 \Rightarrow Electric Circuit

Date 8/08/24

Expt. No. 1.1

Expt. Name To verify KVL

Page No. 1

Experiment 1.1

Aim \Rightarrow To verify Kirchhoff's Voltage Law (KVL)

Apparatus Required \Rightarrow

S.no	Equipment Name	Specifications	Quantity
1	Regulated DC supply	\Rightarrow 0-30V, 0-2A	\Rightarrow 1
2	Digital Multimeter	\Rightarrow 0-30V	\Rightarrow 6
3	Resistor	\Rightarrow of Different values	\Rightarrow 6
4	Connecting wires	\Rightarrow As per requirement	

Theory \Rightarrow

Kirchoff's law are used to determine the current and voltage in different branches of an electric circuit which may not be easily solved by Ohm's law. These laws are applicable to both AC and DC circuits.

Statement of KVL or Mesh Law \Rightarrow

In any closed path (mesh or loop) of an electric circuit, the algebraic sum of product

Teacher's Signature: _____

of current and resistance in each of the conductors plus the algebraic sum of electromotive forces (emfs) in that closed path is zero

$$\text{i.e. } \sum IR + \sum \text{emf} = 0$$

where $IR =$ Potential drop across resistor

$\text{Emf} =$ Potential of battery used in the circuit

$\Sigma =$ algebraic sum

Explanation \Rightarrow

Consider the closed path ABCDA in fig 1.

Different voltage drop will have following signs.

IR_1 is negative (fall in potential)

IR_2 is negative (fall in potential)

E is positive (Rise in potential)

Using KVL, we get,

$$-IR_1 - IR_2 + E = 0 \quad \text{or}$$

$$E = IR_1 + IR_2$$

Voltage rise = Voltage drops

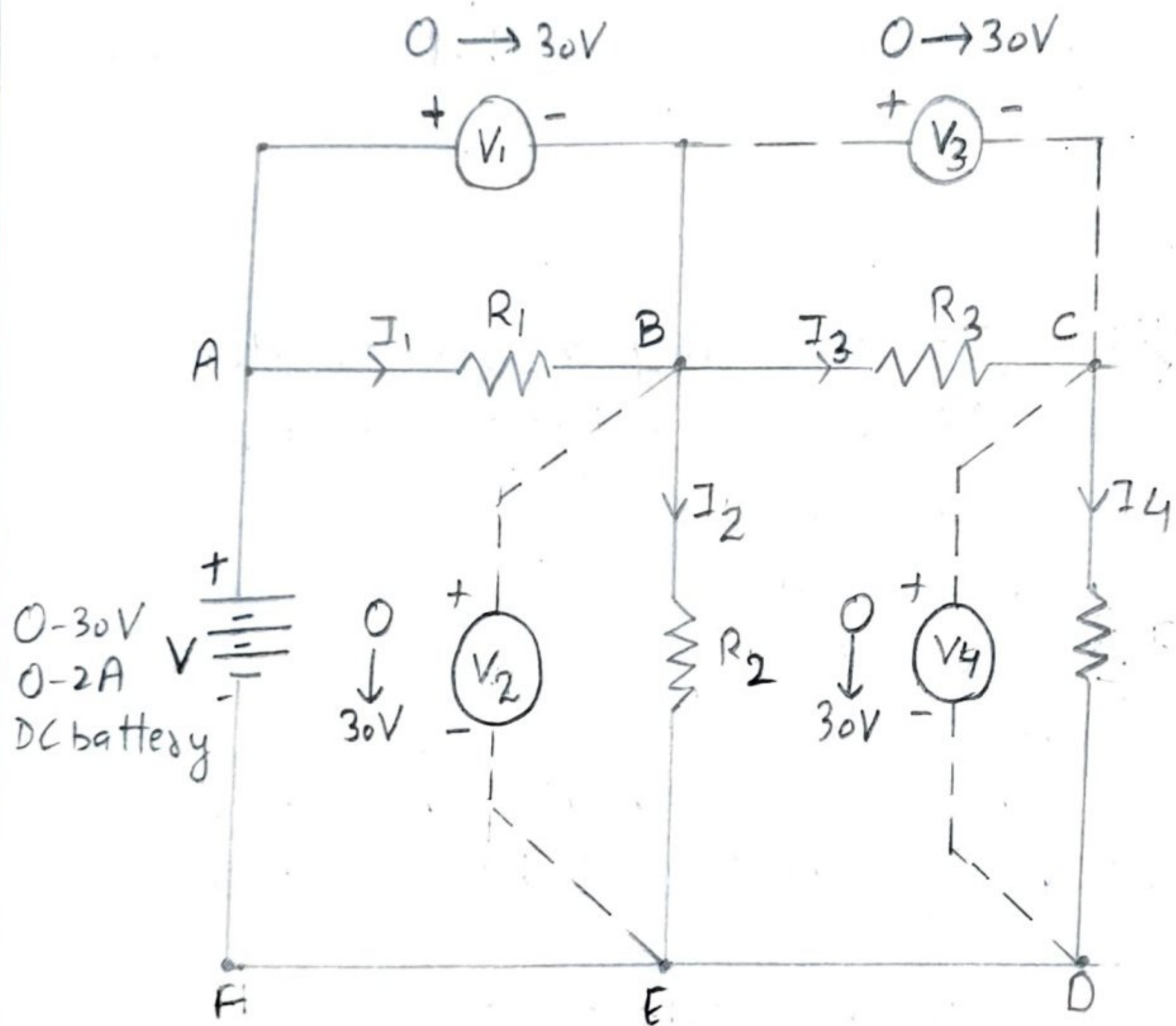


fig 2 circuit diagram of KVL

Limitations \Rightarrow

- 1 Not applicable in stray currents environment and in high frequency applications (even KCL is violated at 60 Hz frequency)
- 2 Not applicable to circuit having distributed elements.

Precautions \Rightarrow

- 1 Switch of the supply first and then start making connections.
- 2 Meters of suitable range should be used as shown

PROCEDURE \Rightarrow

- 1 The circuit is connected as shown.
- 2 The voltage of DC supply was set at 12 V DC supply.
- 3 Different values of R_1 to R_4 were taken and readings of V_1 to V_4 were noted down.
- 4 Accordingly, only one set of reading was taken at 12 V DC supply
- 5 The observations were recording in Table.

Observation Table \Rightarrow

S no.	Voltmeter $V_1(V)$	Voltmeter $V_2(V)$	Voltmeter $V_3(V)$	Voltmeter $V_4(V)$
1				

Result \Rightarrow

S.no	Calculated Values (V)			Theoretical Values (V)		
	$V = V_1 + V_2$	$V_3 = V_2 - V_4$	$V_2 = V_3 + V_4$	$V = V_1 + V_2$	$V_3 = V_2 - V_4$	$V_2 = V_3 + V_4$
1						

Calculations \Rightarrow

- 1
- 2 APPLY KVL IN LOOP ABEF $V = I_1R_1 + I_2R_2$ OR $V = V_1 + V_2$
- 3 APPLY KVL IN LOOP BCDF $V = I_3R_3 + I_4R_4$ OR $V = V_3 + V_4$

Source of Error \Rightarrow

1. Internal resistance of DC battery.
2. Internal resistance of multimeter viz. voltmeter and ammeter
3. Internal resistance of connecting wires.
4. Heating effect of rheostat coil
5. All the sources of error related to multimeter.

Result \Rightarrow

As per Kirchhoff's Voltage Law, the theoretical and calculated values of algebraic sum of emfs and voltage drops are compared as shown

Conclusion \Rightarrow

from Table, the difference in comparison of theoretical and calculated values. The percentage error for $V = V_1 + V_2$, $V_3 = V_2 - V_4$ is found to be _____, _____ and _____. Thus KVL is verified.

Aim \Rightarrow To verify Kirchhoff's Current Law (KCL)

Experiment 1.2

Aim \Rightarrow

To verify Kirchoff's Current Law (KCL)

Apparatus Required \Rightarrow

S.no	Equipment Name	Specifications	Quantity
1	Regulated DC supply	0-30V, 0-2A	1
2	Digital Multimeter	0-2A	6
3	Resistor	of different values	6
4	Connecting wires	As per requirements	


Theory \Rightarrow

Kirchoff's law are used to determine the current and voltage in different branches of an electric circuit which may not be easily solved by Ohm's law. These laws are applicable to both AC and DC circuits.

Statement of KCL or point Law \Rightarrow

It states that the algebraic sum of all the currents meeting at a junction or a node in any electric circuit at any instant is zero.

Fig 3 \Rightarrow Current meeting at a node in KCL

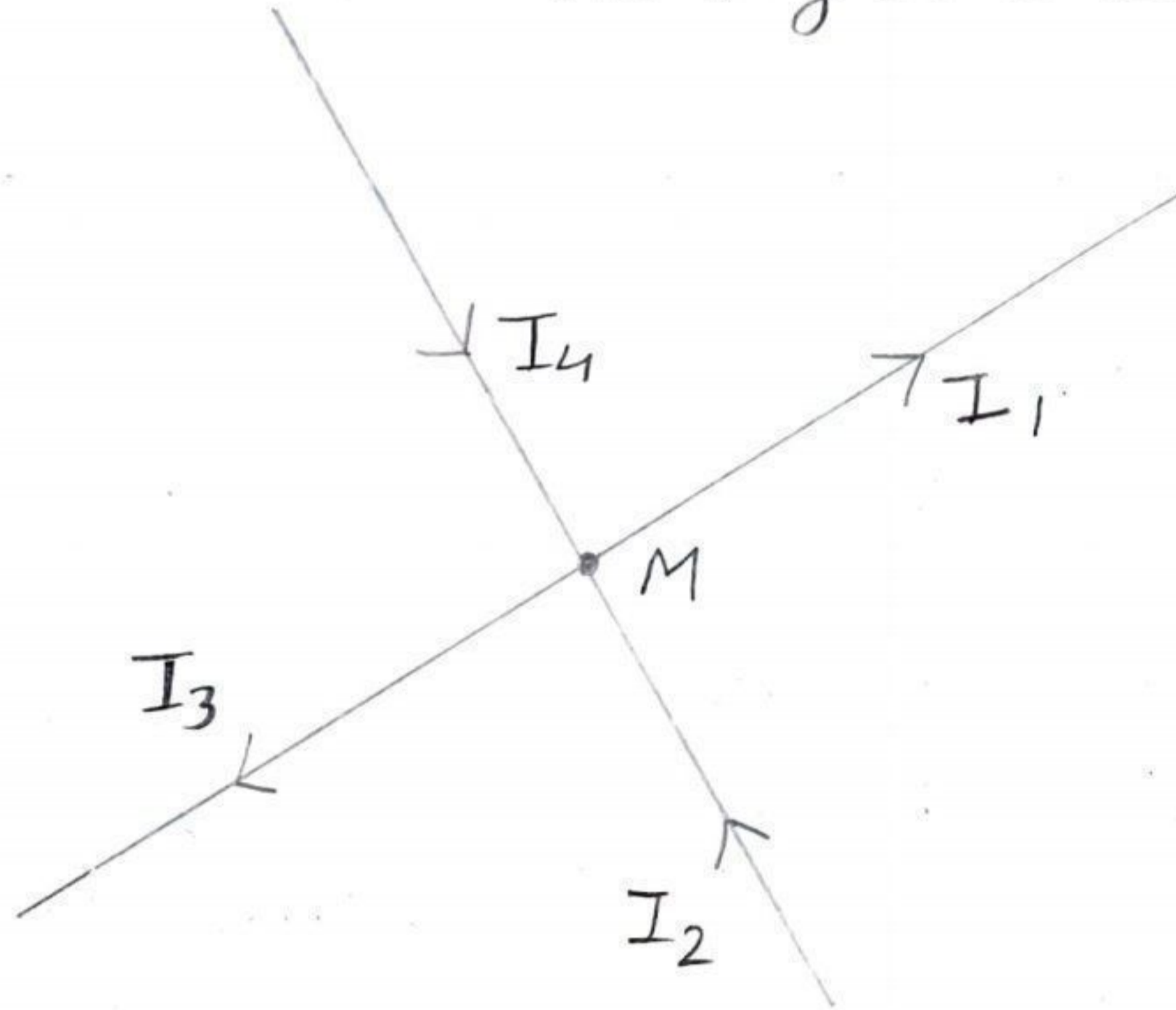

Circuit Diagram \Rightarrow

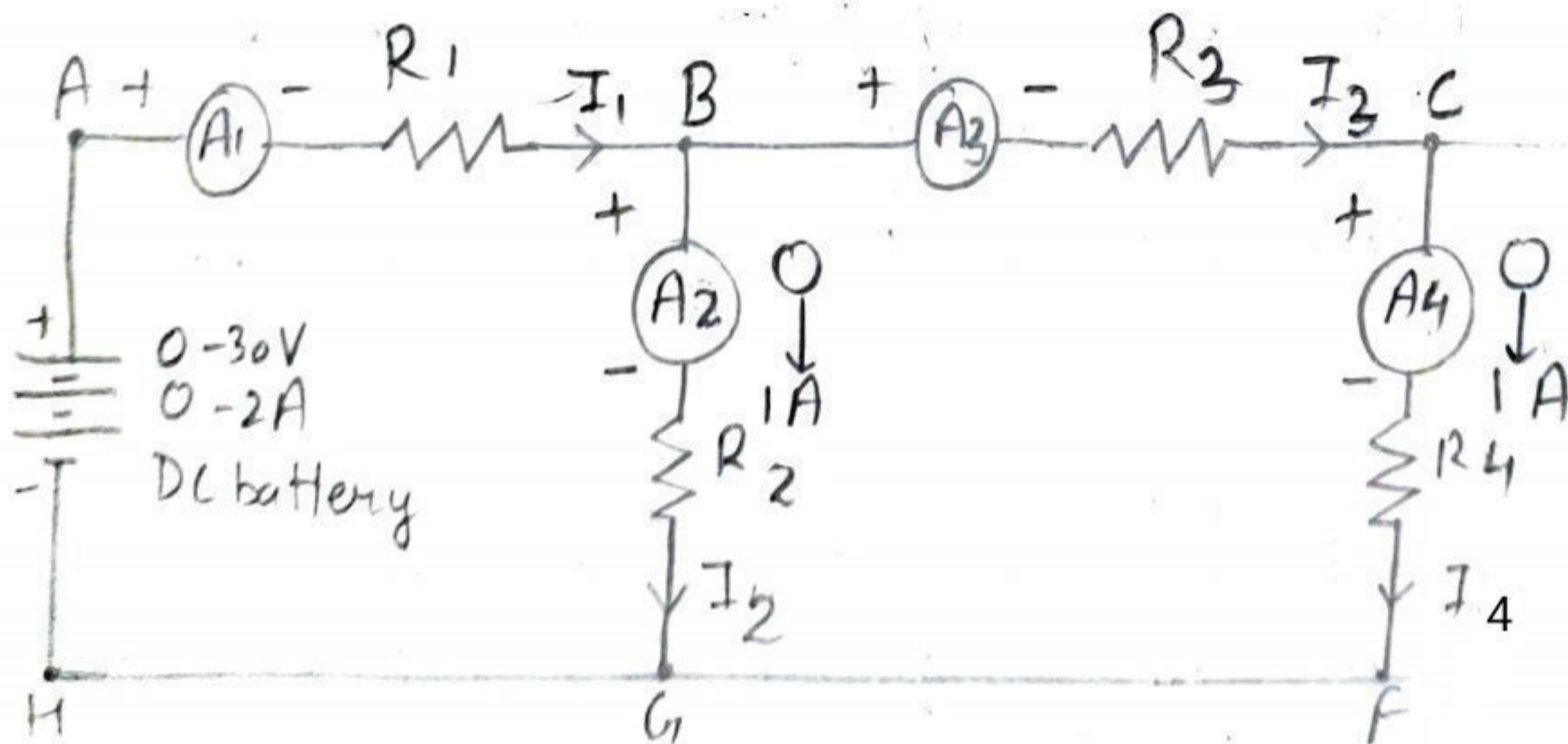


Fig 4 Circuit Diagram of KCL.

Explanation \Rightarrow

Consider that few conductors are meeting at point M as in fig. The arrows indicate the direction of current flow. The currents I_2 and I_4 are coming towards the junction M and I_1 and I_3 are going away from the junction. Assume positive sign for incoming currents and negative sign for outgoing currents.

According to KCL.

$$\sum I = 0$$

$$\text{i.e. } I_2 + I_4 = I_1 + I_3$$

i.e. Incoming currents = Outgoing currents.

Procedure \Rightarrow

- 1 The circuit is connected as shown
- 2 The voltage of DC supply was set at 12V
- 3 Different values of R_1 to R_4 were taken and readings of A_1 to A_4 were noted down.
- 4 Accordingly, only one set of reading was taken at 12V DC supply.
- 5 The observation were recorded in table.

Observation \Rightarrow

Sr no.	Supply Voltage (V)	Ammeter I_1 (A)	Ammeter I_2 (A)	Ammeter I_3 (A)	Ammeter I_4 (A)
1					

Result \Rightarrow

Sr no.	Calculated values (A)	Theoretical values (A)	Percentage error
	$I_1 = I_2 + I_3$ (A)	$I_1 = I_2 + I_3$ (A)	$I_1 = I_2 + I_3$ (A)
1			

Calculations \Rightarrow

1

2

APPLYING KCL AT JUNCTION B, $I_1 = I_2 + I_3$

CALCULATIONS ARE DONE FOR ALL THE READINGS BEING TAKEN USING EQUATIONS TO BE APPLIED AT RESPECTIVE JUNCTION

Result \Rightarrow

As per Kirchhoff's Current law, the theoretical and calculated values of algebraic sum of currents are compared as shown in table.

Conclusion \Rightarrow

The difference in comparison of theoretical and calculated values should be analyzed and resulting difference if any. In both sets of readings is likely due to various sources of errors mentioned in Section. From table, it is seen that errors involved is very small and thus, KCL is verified.